

# Electrical Theory

## Impedance

PJM State & Member Training Dept.

# Objectives




- Identify the components of Impedance in AC Circuits
- Calculate the total Impedance in AC Circuits
- Identify the characteristics of Phase Angles

# Components of Impedance AC Circuits
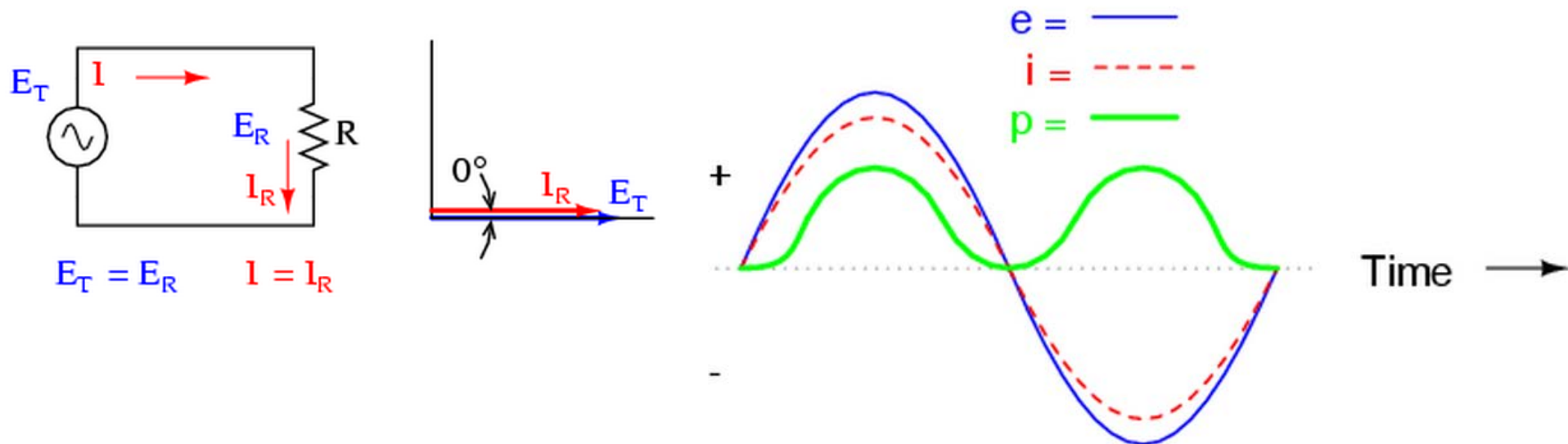
# Resistance

- Resistance:  $R = \frac{E}{I}$
- A change in frequency has no effect on resistance
- Current through a resistor and the voltage drop across the resistor are always in phase



# Resistance Characteristics

- In a purely resistive AC circuit:
  - Voltage and current cycles begin and end at the same time
  - Voltage and current peak values occur at the same time
- Relationship between current and voltage for resistance in an AC circuit is the same as it is in a DC circuit
- Measured values of current and voltage are the Root Mean Square (RMS) values of these quantities
- Only resistance consumes power in a circuit

$$P = E_{RMS} I_{RMS} \cos \theta$$

# Answer Questions 1 and 2

PJM State & Member Training Dept.

# Question 1

A circuit has a 133 ohm resistor connected to a 24 volt source.  
Determine the current flowing in the circuit:

$$E = IR$$


$$a) I = \frac{E}{R} = \frac{24 V}{133 \Omega} = 0.18 \text{ amps}$$

## Question 2

- A stereo receiver has a set of speakers, main and remote, for each channel
  - The speakers for each channel are connected in parallel to the receiver
  - The AC voltage across the speakers is 6.0 volts and the equivalent resistance is  $2.67\Omega$
- Determine the total current supplied by the receiver and the power dissipated in the set of speakers



## Question 2

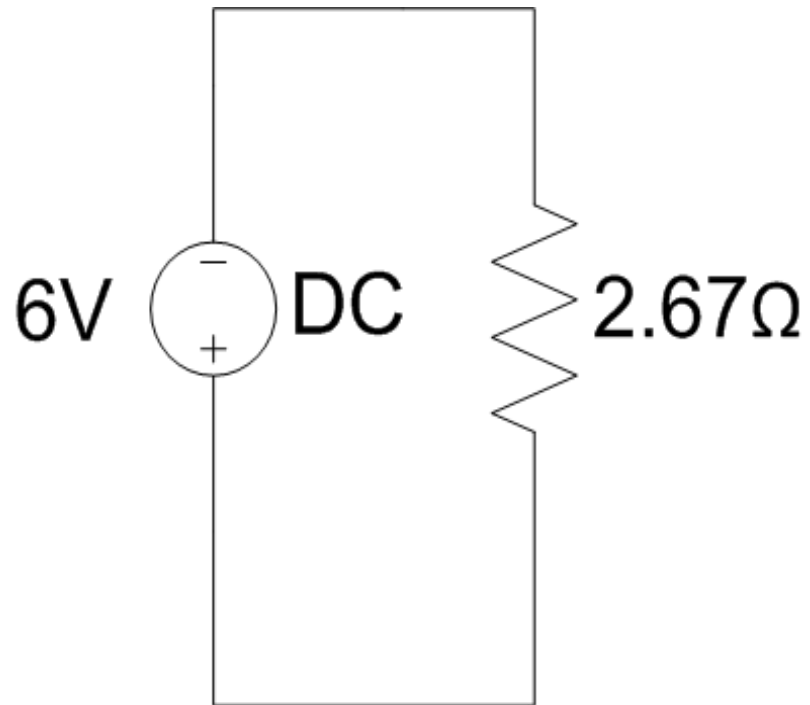

$$I_T = \frac{E_S}{R_T} = \frac{6\text{ V}}{2.67\ \Omega} = 2.25\ \text{amps}$$

$$P_T = (6\text{ V})(2.25\ \text{amps}) = 13.5\ \text{watts}$$

# Inductive Reactance Characteristics

- An inductor's basis of operation is Faraday's law of electromagnetic induction
- An inductor develops a voltage that opposes a change in current
- Does not convert electrical energy into heat energy

# Inductive Reactance Characteristics

- It is the result of induced voltage in a coil by the moving magnetic field created by current flow
- Current must be changing for voltage to be induced
- An inductor allows just enough current flow to produce a voltage equal to but opposing the source voltage
- Inductive reactance ( $X_L$ ) is measured in ohms and determines how much RMS current exists in an inductor for a given RMS voltage across the inductor

# Inductive Reactance

- Average power and average energy used by a inductor in an AC circuit is zero
  - a) When the voltage and current product is positive, the inductor is returning energy
  - b) When the voltage and current product is negative, energy is delivered to the inductor

# Inductive Reactance

- Ohm's Law and inductive reactance:

$$E = (I)(X_L) \quad X_L = 2\pi fL$$

*where,*

E and I = RMS values for voltage and current


f = frequency (hertz)

L = inductance (henry)

- Increasing frequency increases inductive reactance
- As frequency increases, current changes more rapidly increasing the value of induced voltage
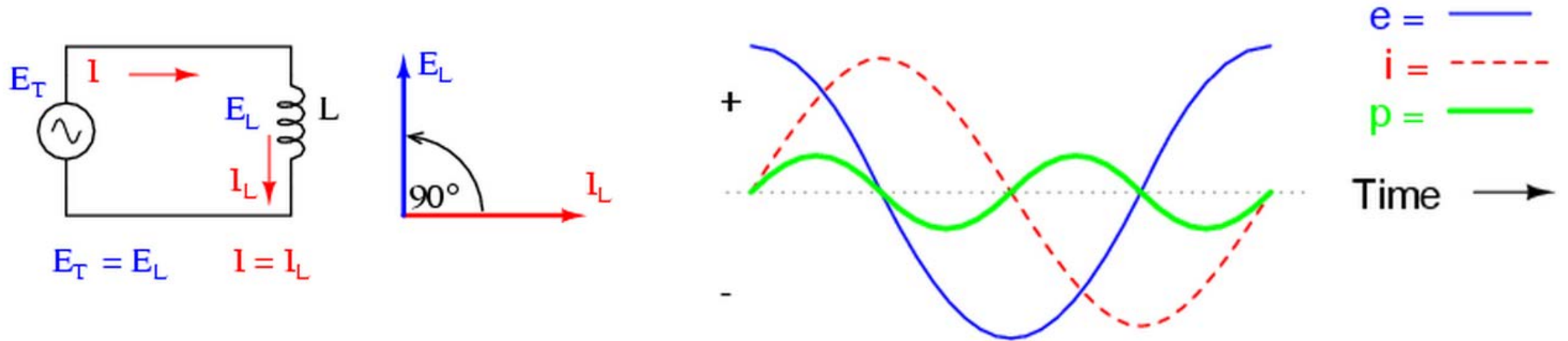
# Inductive Reactance

In a purely inductive circuit, voltage leads the current by 90 degrees



# Answer Questions 3-6

PJM State & Member Training Dept.

## Question 3

Calculate the inductive reactance of a circuit having a pure inductance of 50 millihenries with a frequency of 60 Hz

$$X_L = 2\pi fL = 2\pi(60 \text{ Hz})(0.05 \text{ H}) = 18.85 \Omega$$



## Question 4

Calculate the inductive reactance of a 2 henry inductance at 60 Hz

$$X_L = 2\pi fL$$

$$X_L = 2\pi(60)(2)$$

$$X_L = 754 \Omega$$

## Question 5

A 0.16 H inductor is wired across the terminals of a generator that has a voltage of 120 volts and supplies a current of 5 amps

What is the frequency of the generator?

$$X_L = \frac{E}{I} = \frac{120 \text{ V}}{5 \text{ A}} = 24 \Omega$$

$$X_L = 2\pi fL$$

$$24 \Omega = 2\pi f(0.16 \text{ H})$$

$$f = \frac{24 \Omega}{2\pi(0.16 \text{ H})} = \frac{24 \Omega}{1.005} = 23.88 \text{ Hz}$$

## Question 6

An 8.2 mH inductor is connected to an AC generator that is operating at 10.0 V and 60 Hz

What is the current supplied by the generator?

$$X_L = 2\pi fL = 2\pi(60 \text{ Hz})(0.0082 \text{ H}) = 3.09 \Omega$$

$$I_P = \frac{E}{X_L} = \frac{10 \text{ V}}{3.09 \Omega} = 3.24 \text{ A}$$

# Capacitive Reactance

- Ohm's Law and capacitive reactance:  $I = \frac{E}{X_C}$      $X_C = \frac{1}{2\pi f C}$

*where,*

E and I = RMS values for voltage and current

f = frequency (hertz)

C = capacitance (farads)

- Increasing frequency decreases capacitive reactance
- As frequency decreases, capacitive reactance becomes infinitely large, and a capacitor provides so much opposition to the motion of charges that there is no flow of current

# Capacitive Reactance Characteristics




- In an AC circuit containing a capacitor, the polarity of the voltage continually reverses switching back and forth with the electrical charges also surging back and forth
- This constitutes an alternating current with charge flowing continuously
- A capacitor controls the current in an AC circuit by storing energy that produces voltage in a capacitor
- Capacitive reactance ( $X_C$ ) is measured in ohms and determines how much RMS current exists in a capacitor in response to a given RMS voltage across the capacitor

# Capacitive Reactance Characteristics

- Does not convert electrical energy into heat energy
- It is the result of the capacitor storing energy that produces a voltage that opposes the source voltage and controls current
- Average power and average energy used by a capacitor in an AC circuit is zero
  - a) When the voltage and current product is positive, energy is delivered to the capacitor
  - b) When the voltage and current product is negative, the capacitor is returning energy
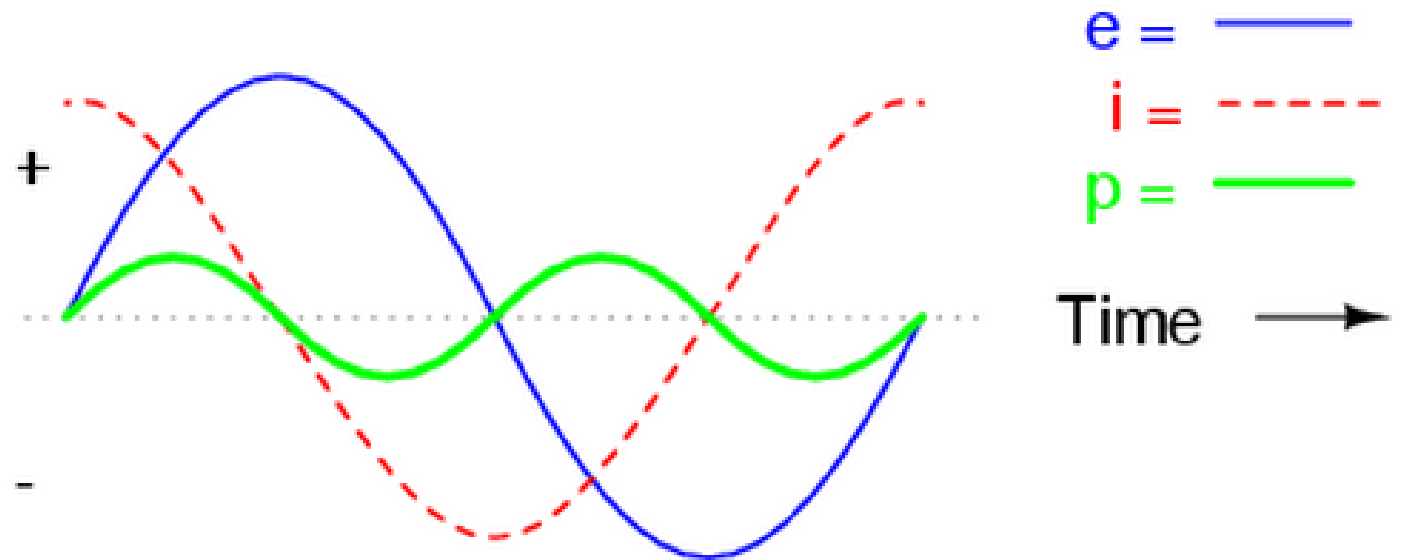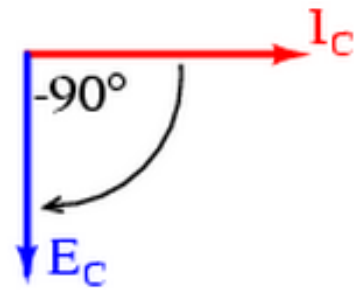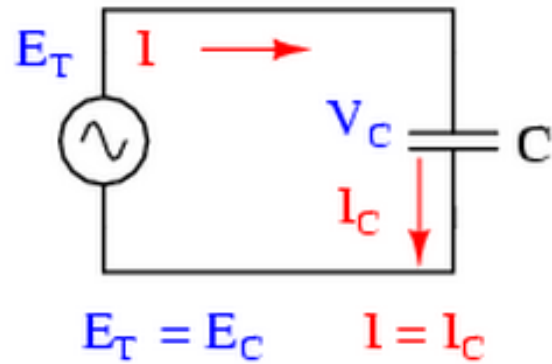
# Capacitive Reactance

- In a purely capacitive circuit, current leads the voltage by 90 degrees



# Capacitive Reactance

- Capacitors are used by utilities for:
  - Voltage regulation
  - Power factor correction
  - Inductance reduction
  - Measuring devices for protection systems
  - Communications for power line carriers
  - Filters for undesirable high frequency signals



# Answer Questions 7-9

PJM State & Member Training Dept.

## Question 7

Calculate the capacitive reactance of a circuit having a capacitor of 400 microfarads with a frequency of 60 Hz

$$X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi(60 \text{ Hz})(0.0004 \text{ F})} = 6.63 \Omega$$

## Question 8

- In a circuit, the capacitance of a capacitor is 1.65 microfarads, and the rms voltage of the generator is 50 volts
- What is the rms current in the circuit when the frequency is (a) 200 Hz and (b) 4500 Hz?

$$a) X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(200 \text{ Hz})(0.00000165 \text{ F})} = 482.3 \Omega$$

$$I_{RMS} = \frac{E_{RMS}}{X_C} = \frac{50 \text{ V}}{482.3 \Omega} = 0.104 \text{ A}$$

$$b) X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(4500 \text{ Hz})(0.00000165 \text{ F})} = 21.44 \Omega$$

$$I_{RMS} = \frac{E_{RMS}}{X_C} = \frac{50 \text{ V}}{21.44 \Omega} = 2.33 \text{ A}$$

## Question 9

Calculate the current through a 1 μfarad capacitor, the effective value of voltage applied across the capacitor is 100 volts, and the frequency is 60 Hz

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(60 \text{ Hz})(0.000001 \text{ F})} = 2652.6 \Omega$$

$$I = \frac{E}{X_C} = \frac{100 \text{ V}}{2652.6 \Omega} = 0.0377 \text{ A}$$

# LabVolt Exercises

- Do LabVolt exercises 1.1, 1.2, 3.1, 3.3, 4.1 and 4.3

# Total Impedance AC Circuits

# Total Impedance

- The impedance ( $Z$ ) of an AC circuit is a complex sum of resistance ( $R$ ) and net reactance ( $X_L - X_C$ )
- Impedance usually represented in polar form, with a magnitude and an angle ( $Z \angle \theta$ )
- Impedance is the total opposition to the flow of charge in an AC circuit
- A right triangle, called the impedance triangle is used to illustrate the relationship between AC resistance, reactance, and impedance

# Total Impedance

- Impedance (Z) is measured in ohms and defined as:  $Z = \sqrt{R^2 + X_T^2}$

*Where:*

$$X_T = X_L - X_C$$

R = Resistance

$X_T$  = Total Reactance


$X_L$  = Inductive Reactance

$X_C$  = Capacitive Reactance

- $X_L$  and  $X_C$  are 180° out of phase



# Total Impedance

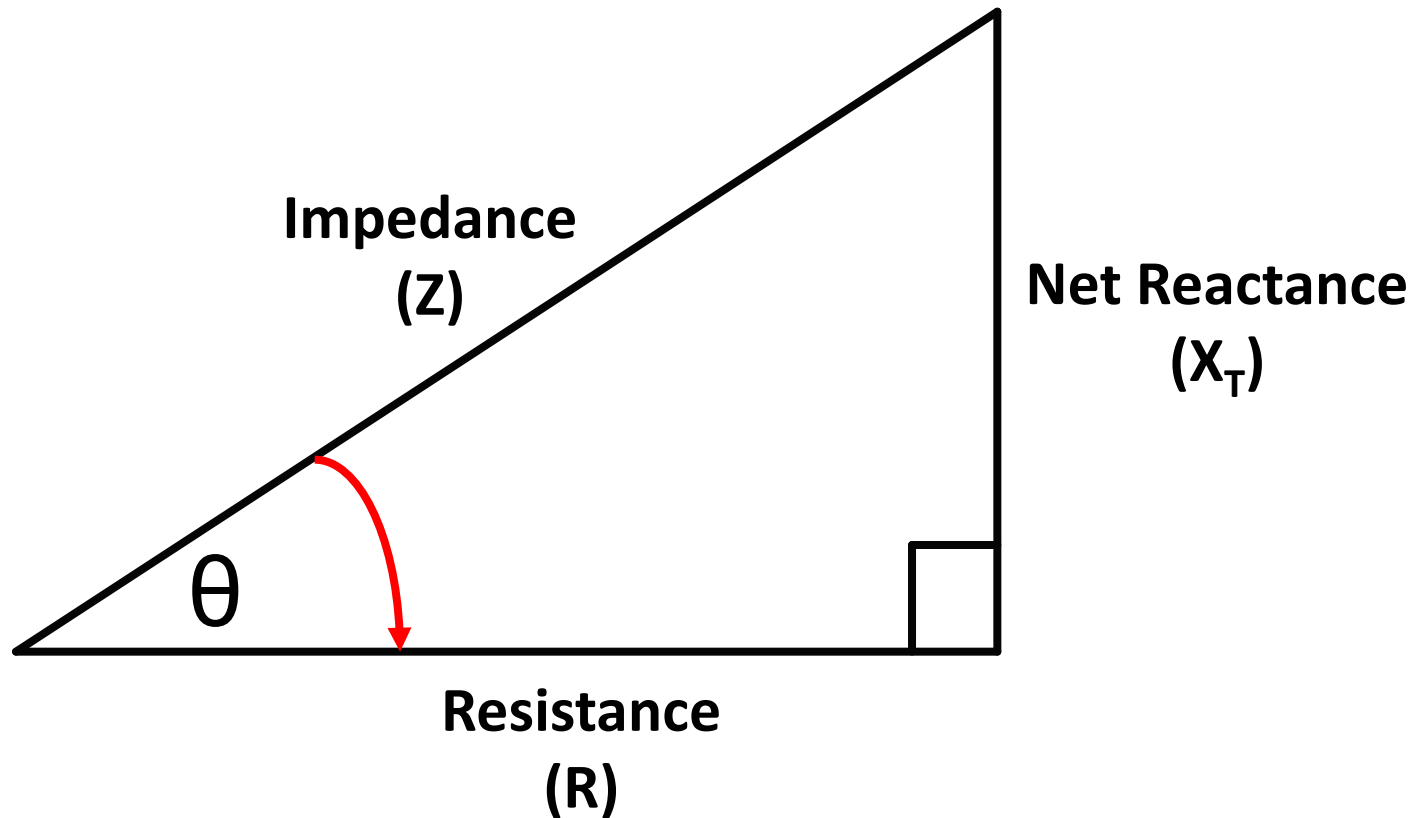

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \frac{R}{\cos \theta}$$

$$Z = \frac{X_T}{\sin \theta}$$

# Answer Questions 10 and 11

PJM State & Member Training Dept.

## Question 10

Given a RL circuit with a resistance of 5 ohms and a 35 ohm inductance at 60 Hz AC, find the (a) impedance (Z) and, (b) angle theta

$$a) Z = \sqrt{R^2 + X_T^2} = \sqrt{5^2 + 35^2} = \sqrt{1444.78} = 35.36 \Omega$$

$$\cos \theta = \frac{R}{Z}$$

$$b) \theta = \cos^{-1} \frac{R}{Z} = \cos^{-1} \frac{5 \Omega}{35.36 \Omega} = \cos^{-1}(0.1414) = 81.87^\circ$$

## Question 11

Given a RLC circuit where  $R$  is 5 ohms,  $X_L = 35$  ohms, and  $X_C$  is 15 ohms, find the (a) impedance and (b) the angle theta


$$X_T = X_L - X_C = 35 \Omega - 15 \Omega = 20 \Omega$$

$$a) Z = \sqrt{R^2 + X_T^2} = \sqrt{5^2 + 20^2} = \sqrt{425} = 20.62 \Omega$$


$$b) \theta = \cos^{-1} \frac{R}{Z} = \cos^{-1} \frac{5 \Omega}{20.62 \Omega} = \cos^{-1} 0.2425 = 75.97^\circ$$
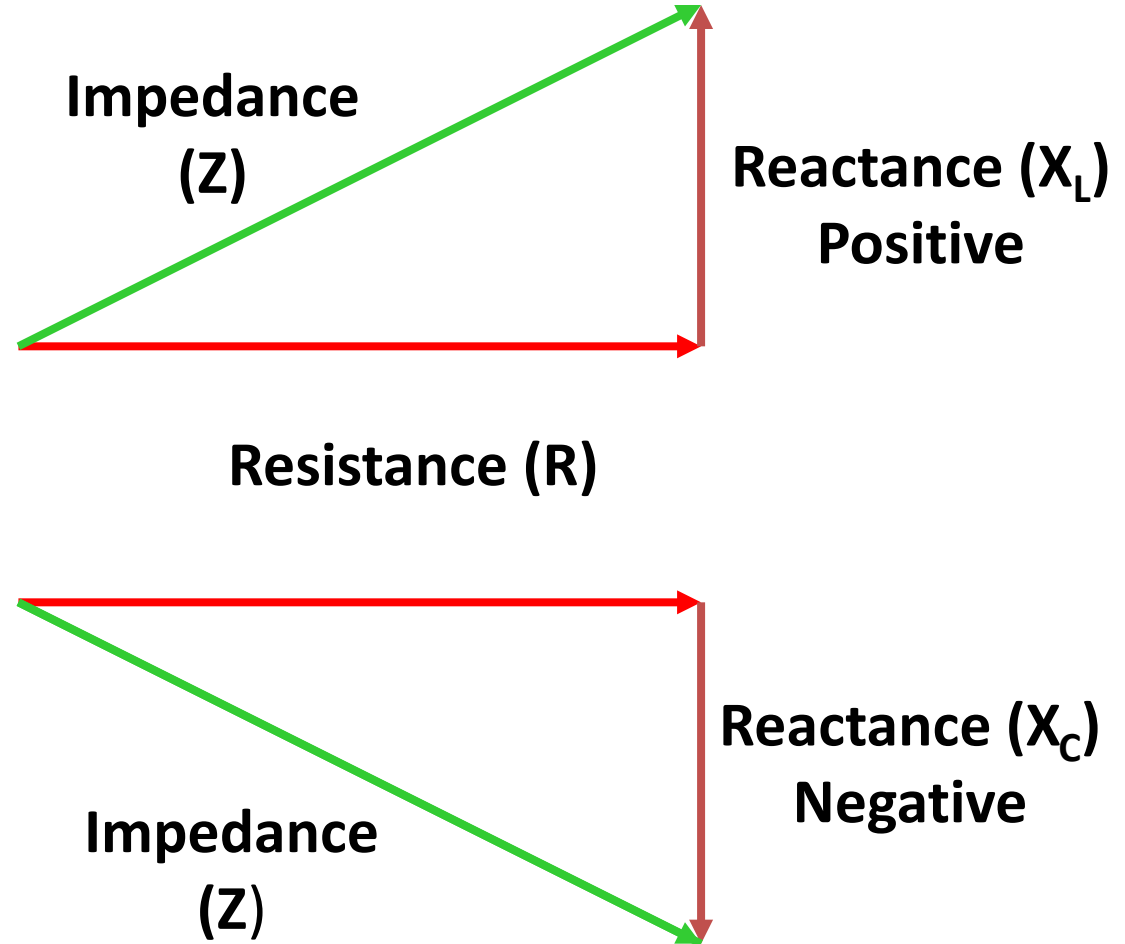
# Total Impedance


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
$$Z = \frac{R}{\cos \theta}$$
$$Z = \frac{X_T}{\sin \theta}$$



# Total Impedance


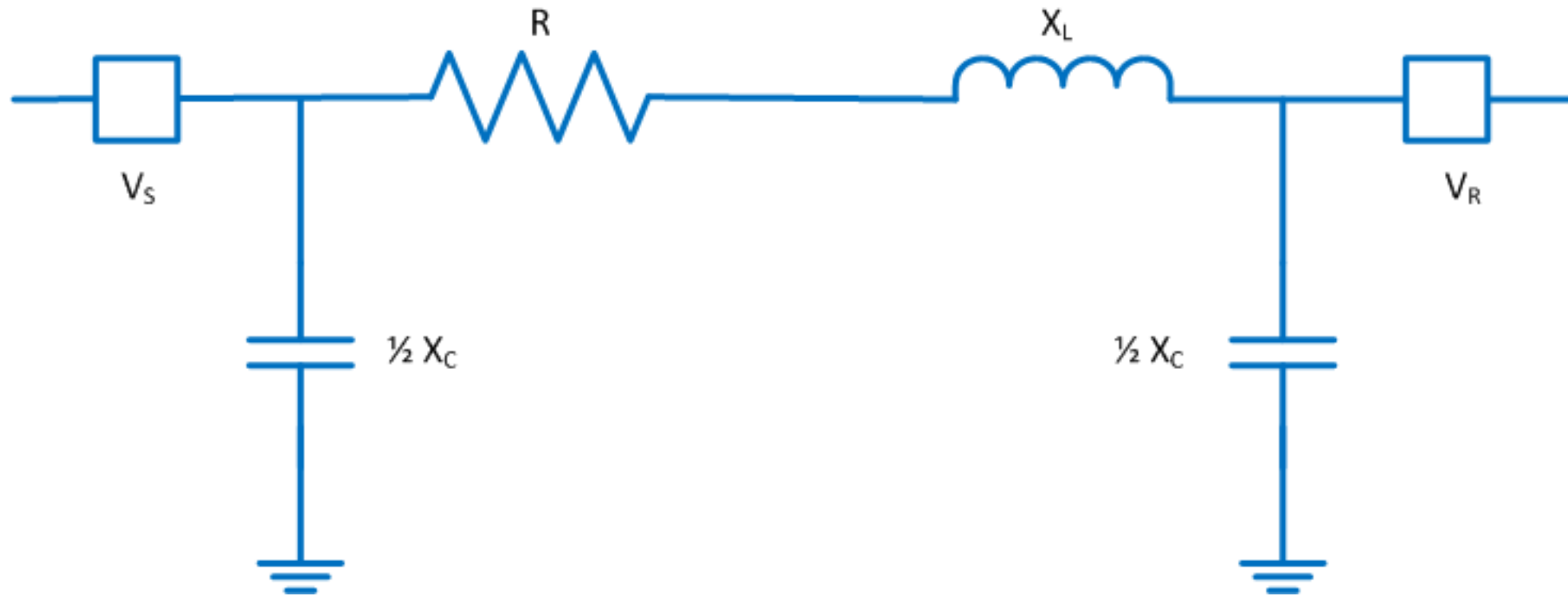


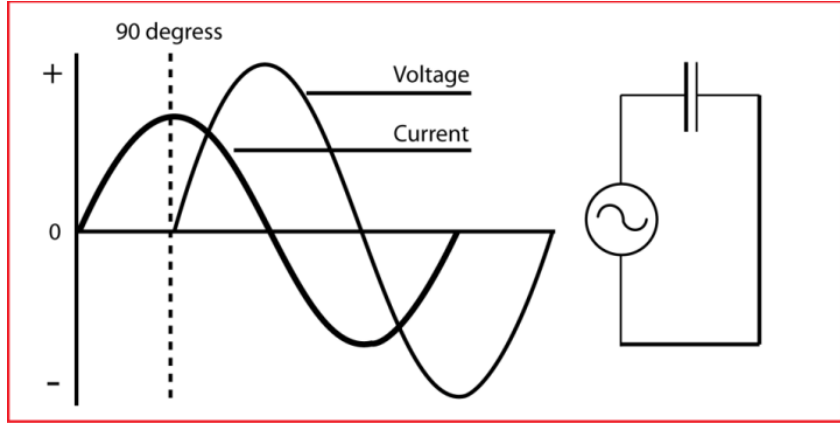**Values will depend on a line's length, cross-sectional area,  
and conductor spacing**





# Phase Angle

## Part 3

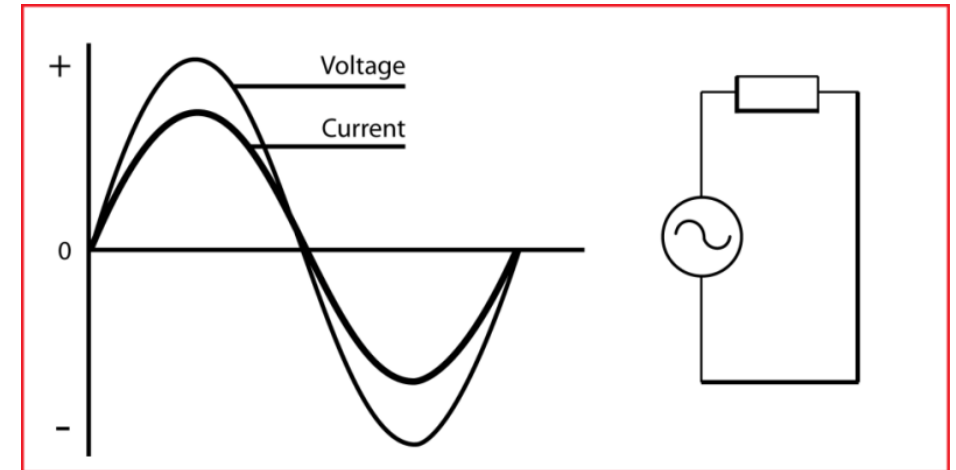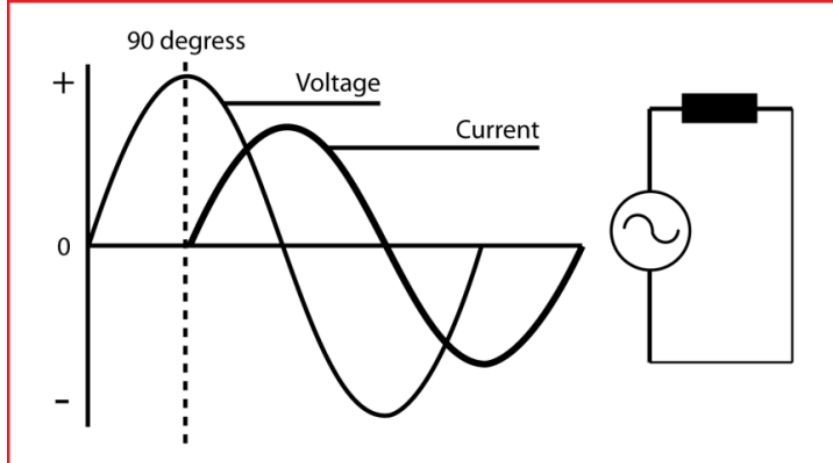
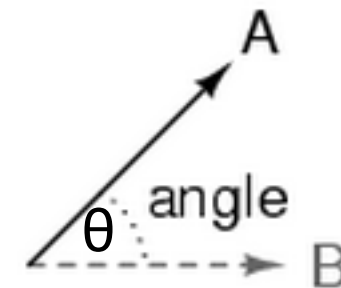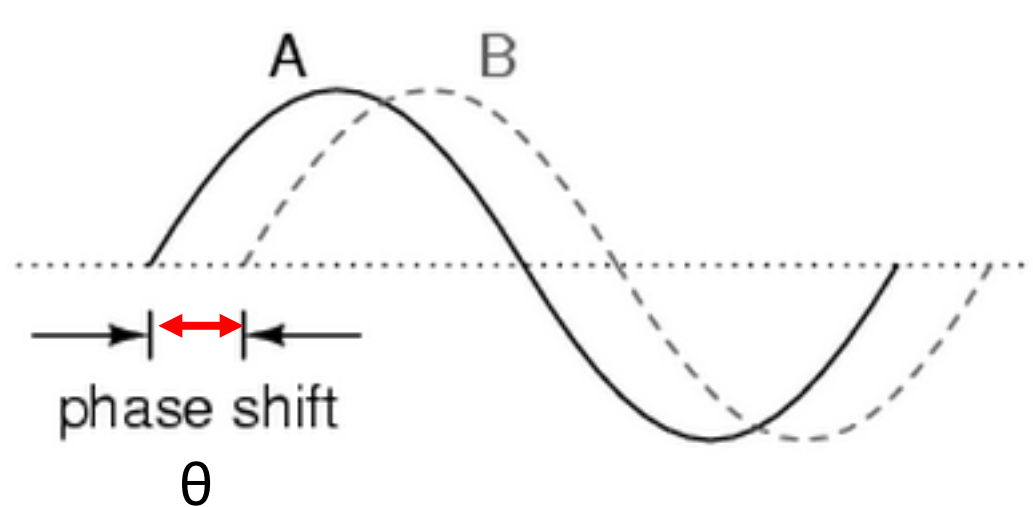
# Phase Angle


- Phase angle is defined as the angular separation between two phasors
- The spacing between the zero crossings of two waveforms also illustrates the phase angle ( $\theta$ ) of the circuit





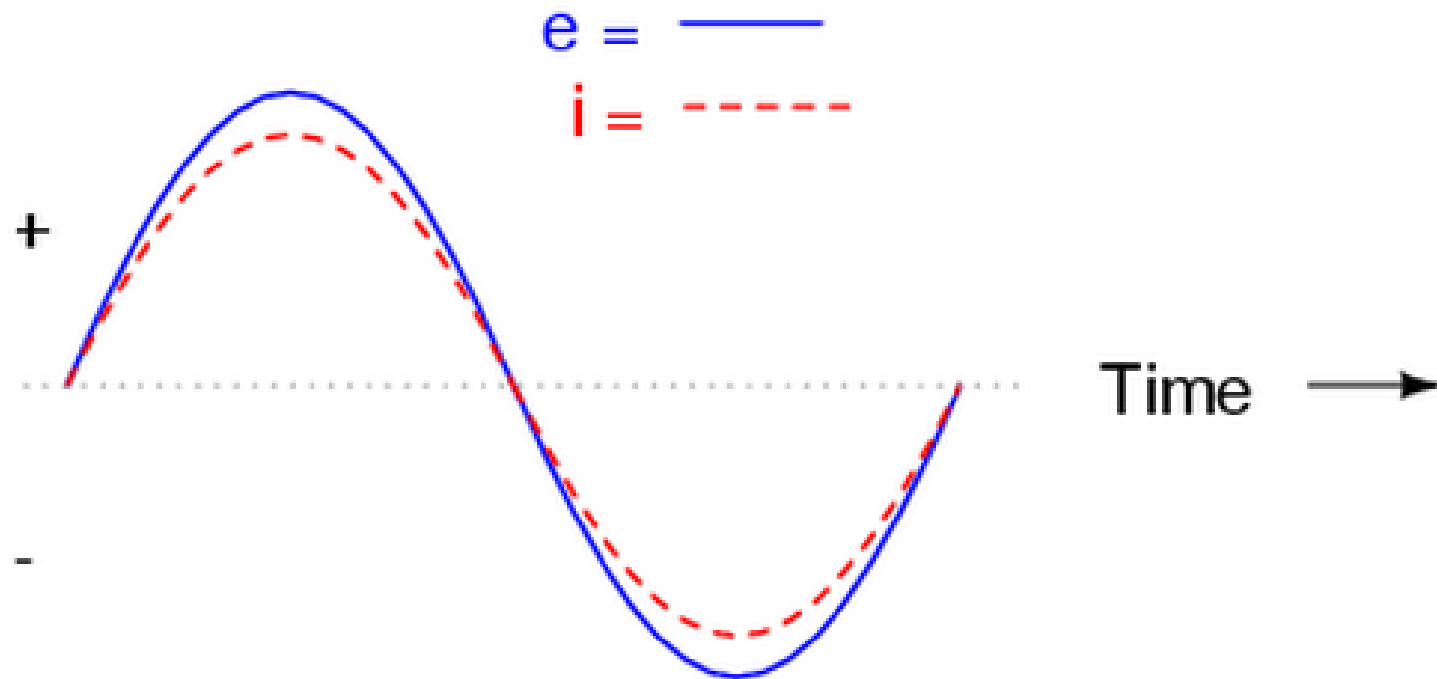
# Phase Angle

- The phase angle of a circuit is directly related to the impedance of the circuit
- For a purely resistive circuit, voltage and current will be in phase, and the phase angle will be zero



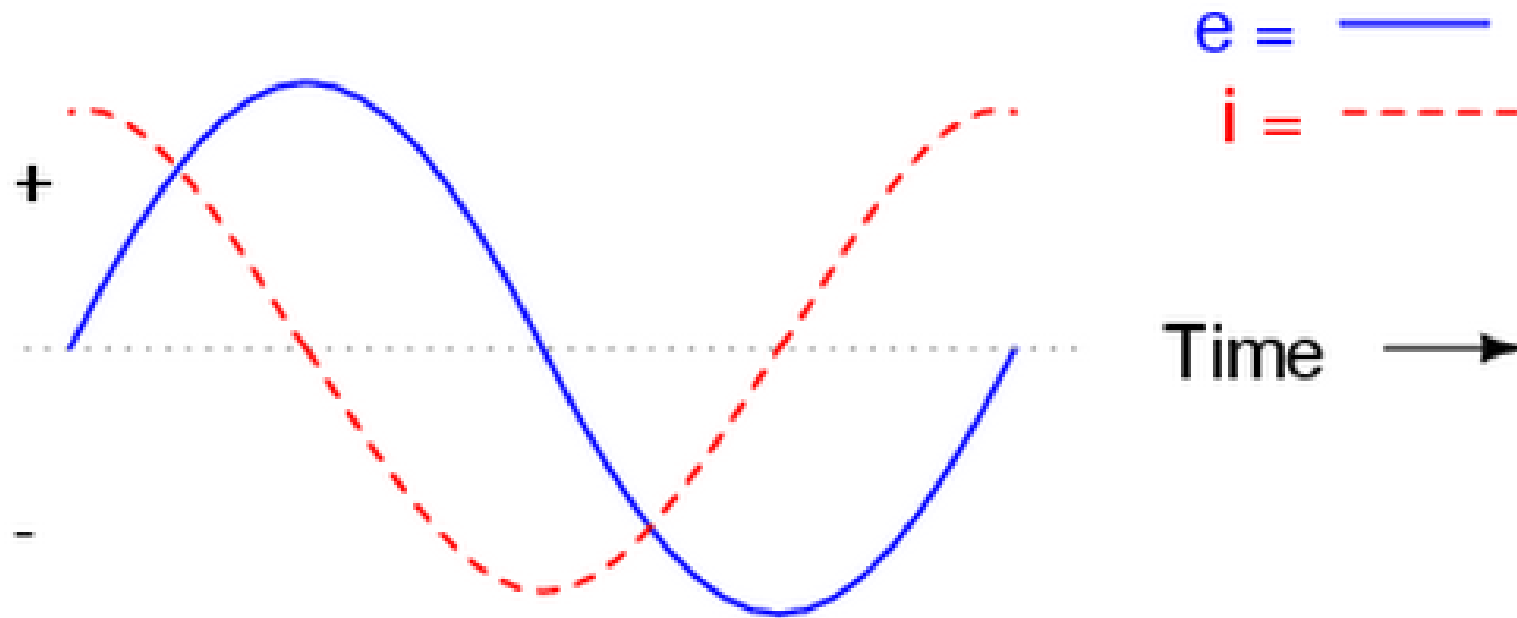
# Phase Angle

- A circuit has a leading phase angle when the current wave leads the voltage wave
- This occurs when the circuit is predominantly capacitive because of the energy storage of the electric field


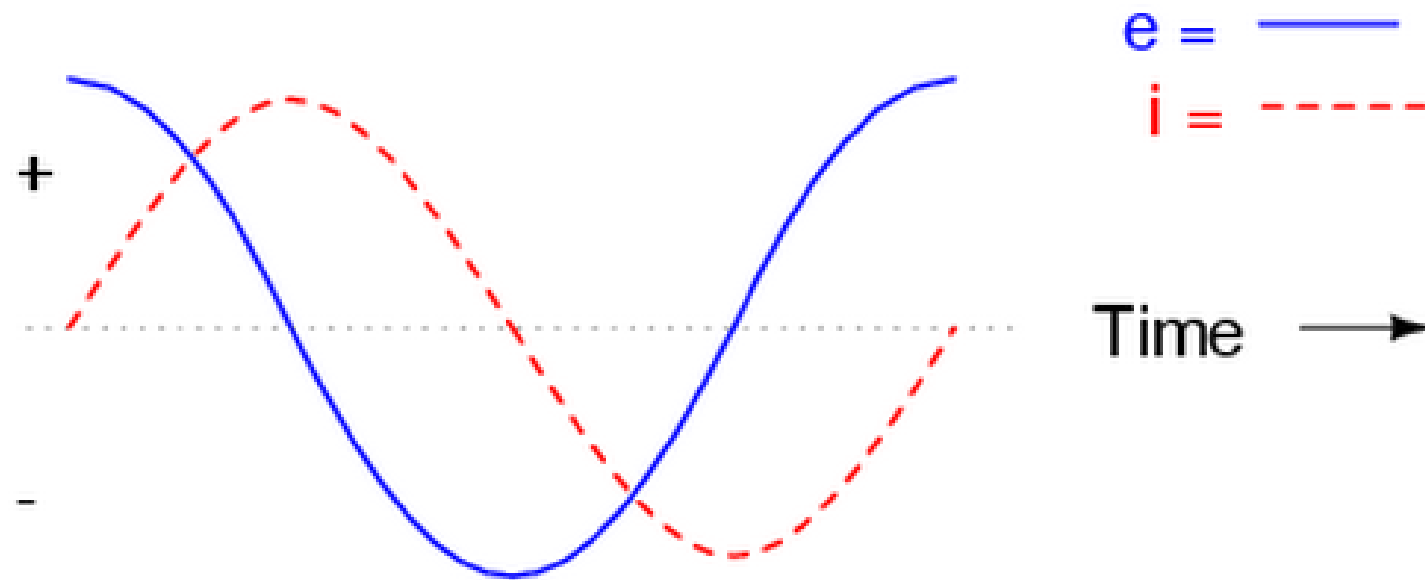
# Phase Angle

- A circuit has a lagging phase angle when the current wave lags behind the voltage wave
- This occurs when the circuit is predominantly inductive because of the energy storage of the magnetic field



# Summary

- Identified the components of Impedance in AC Circuits
- Calculated the total Impedance in AC Circuits
- Identified the characteristics of Phase Angles

# Contact Information

**PJM Client Management & Services**

**Telephone: (610) 666-8980**

**Toll Free Telephone: (866) 400-8980**

**Website: [www.pjm.com](http://www.pjm.com)**



The Member Community is PJM's self-service portal for members to search for answers to their questions or to track and/or open cases with Client Management & Services

# LabVolt Exercises

Do LabVolt exercises **5.2** and **5.4**